
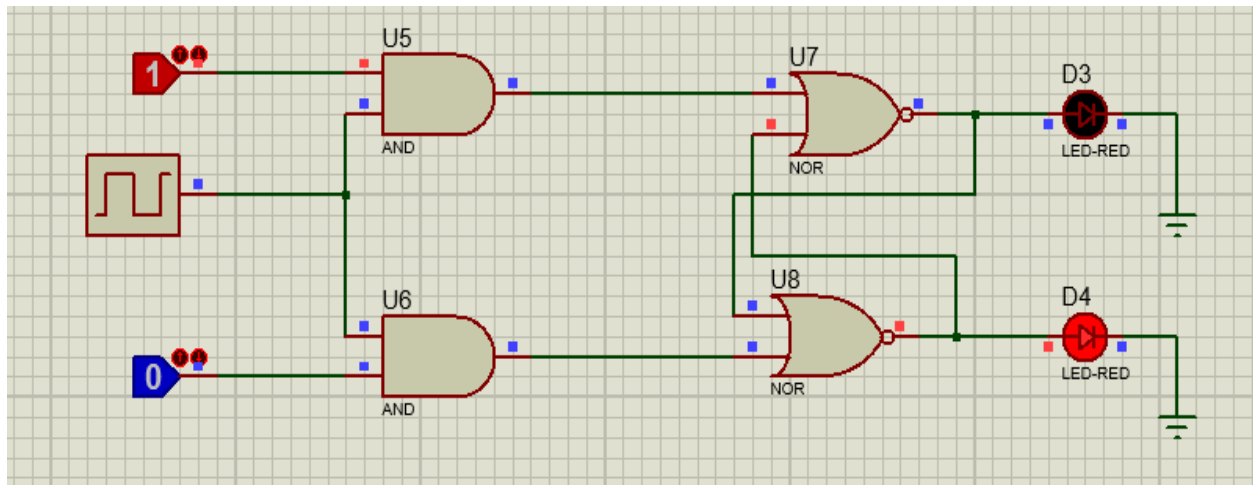



S-R Flip-Flip

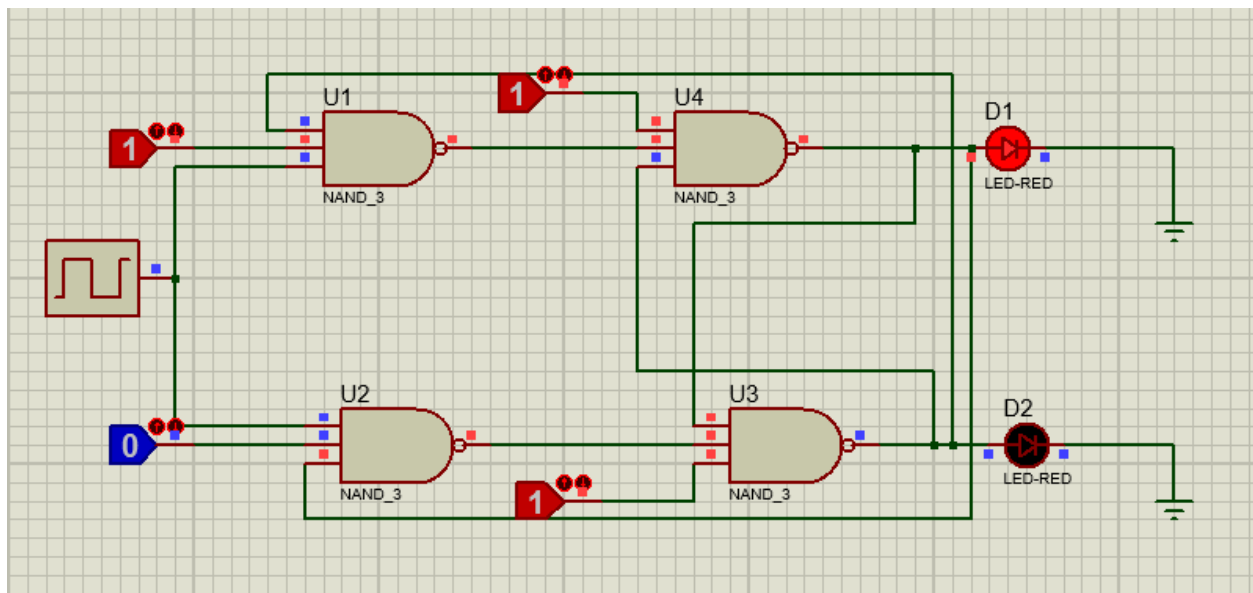


J-K Flip-flop




D Flip-Flop

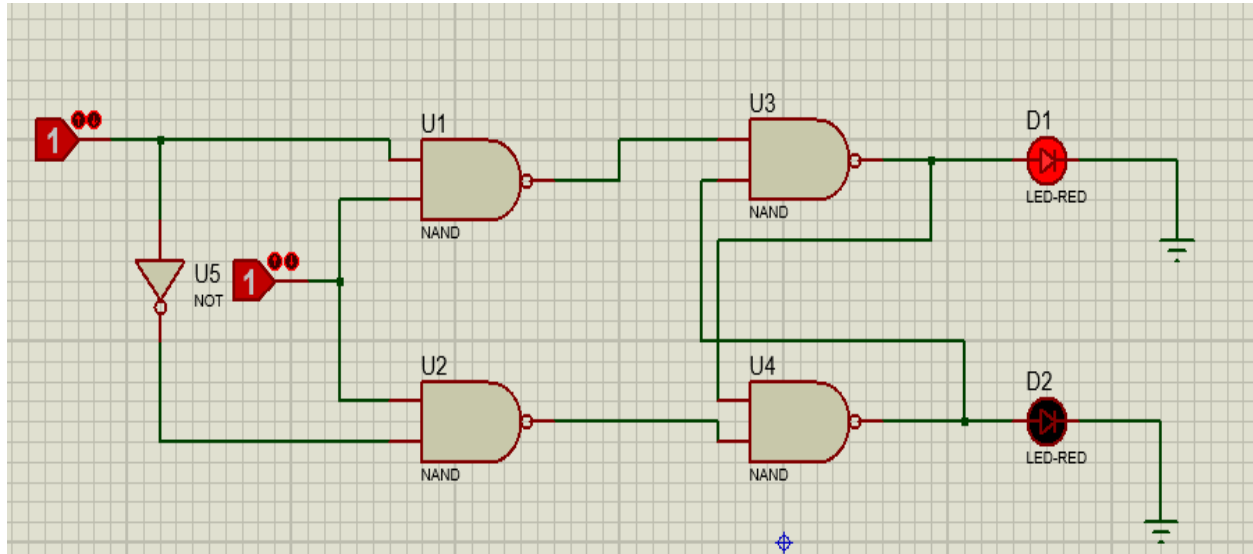


T Flip-Flop

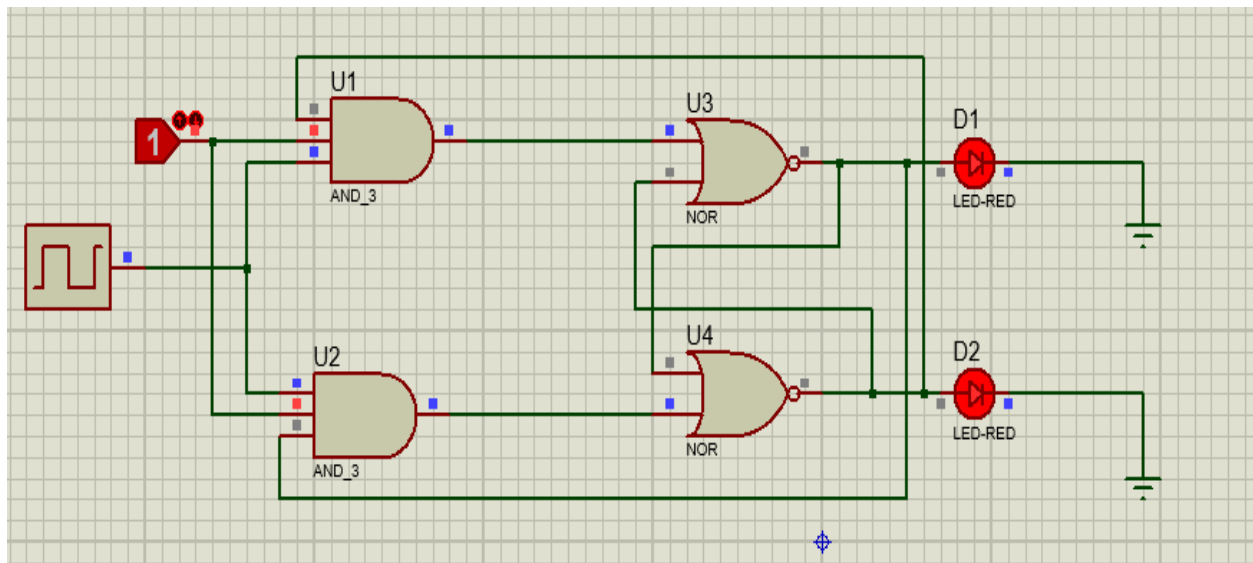


Encoder

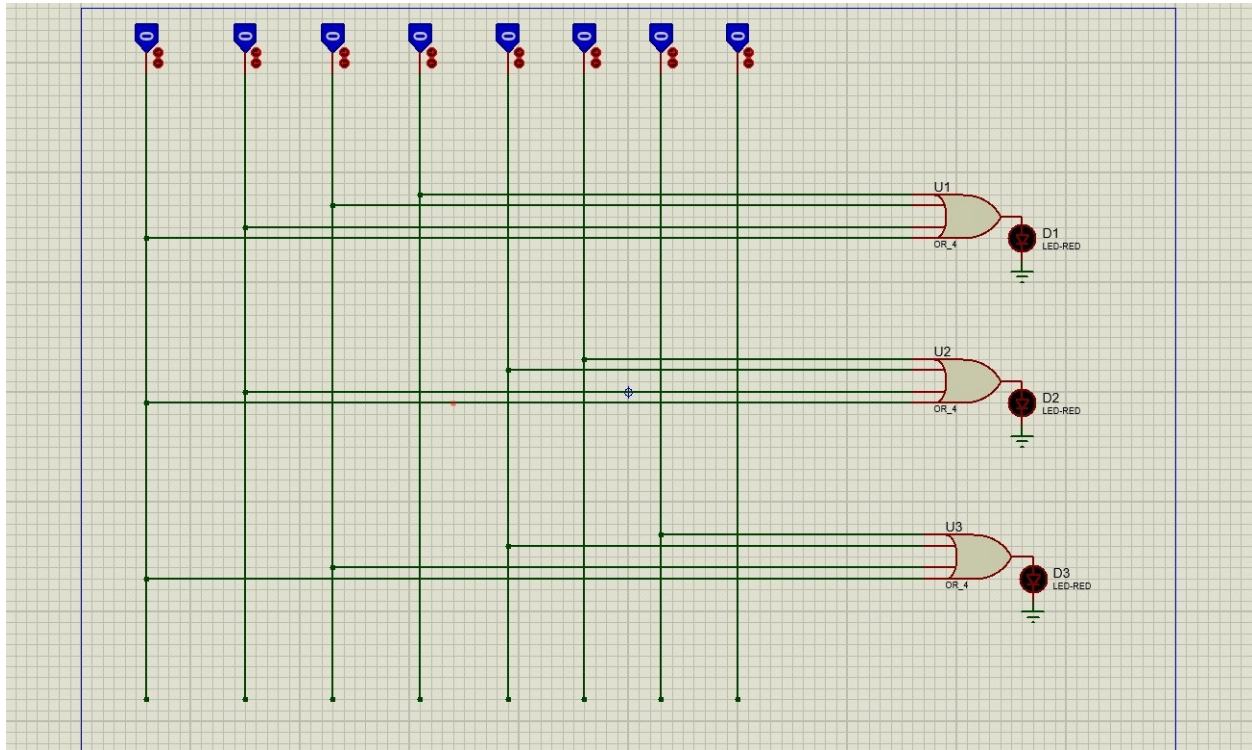


Down Counter

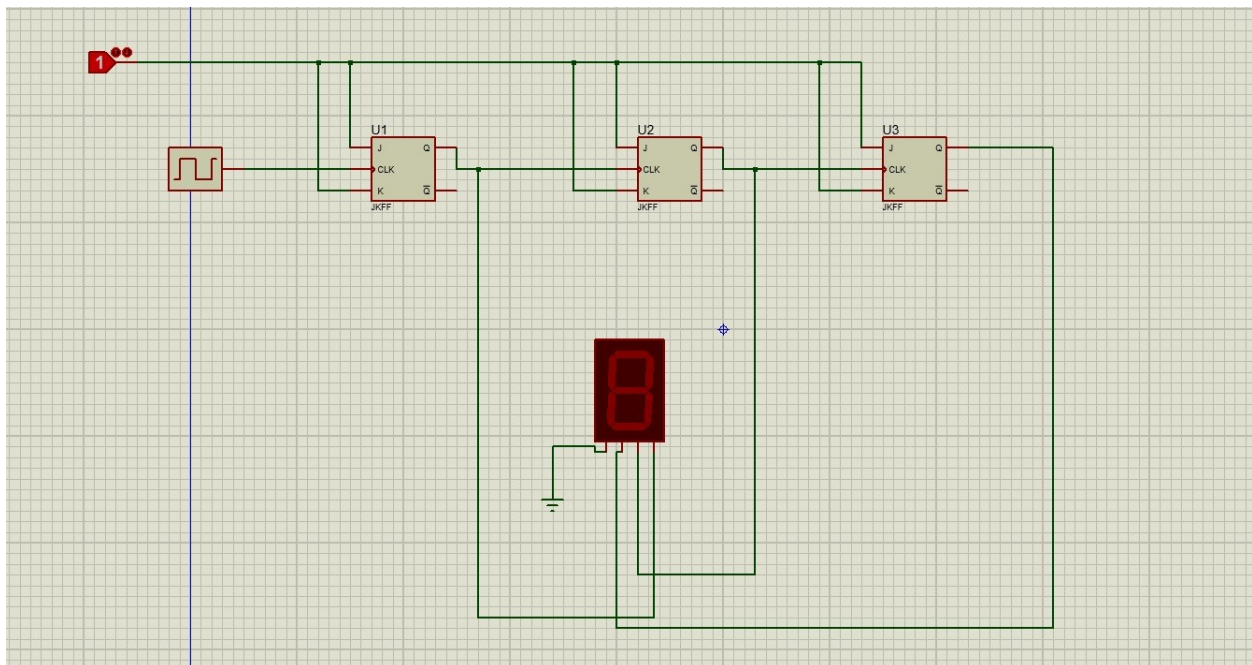


DeMux

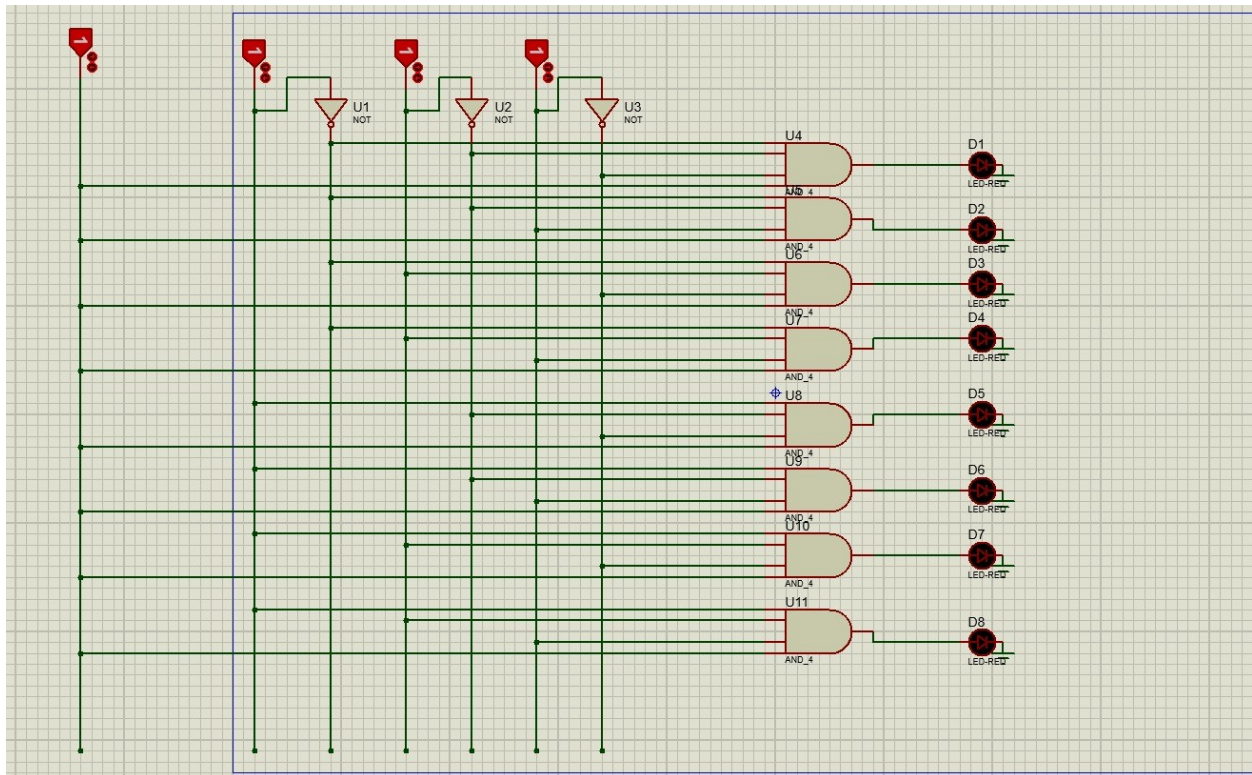


Up Counter

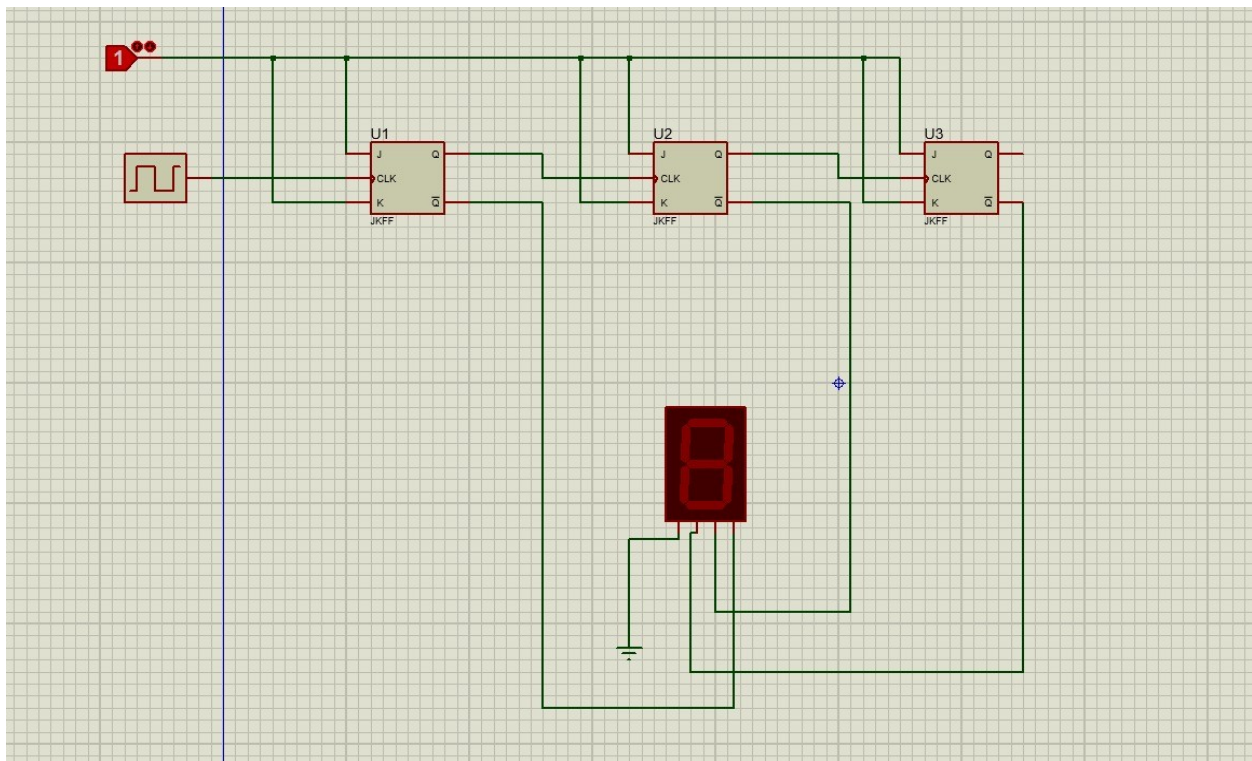


Implementation of Mux

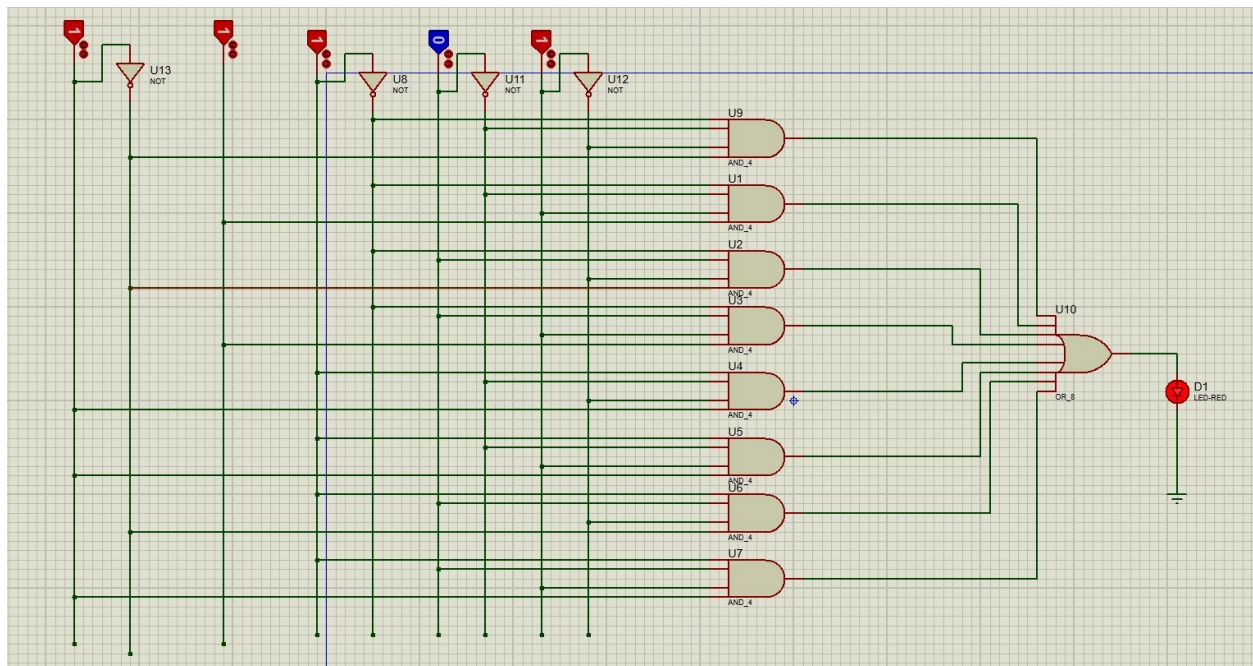

Mux

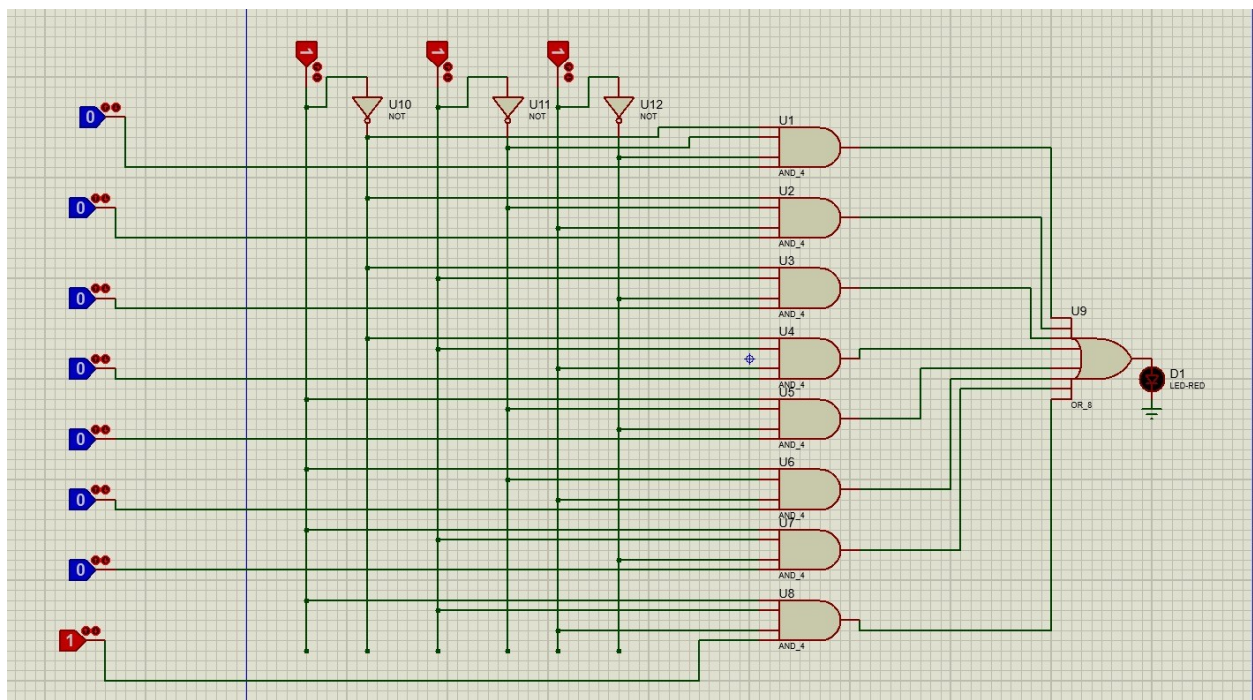

Decoder

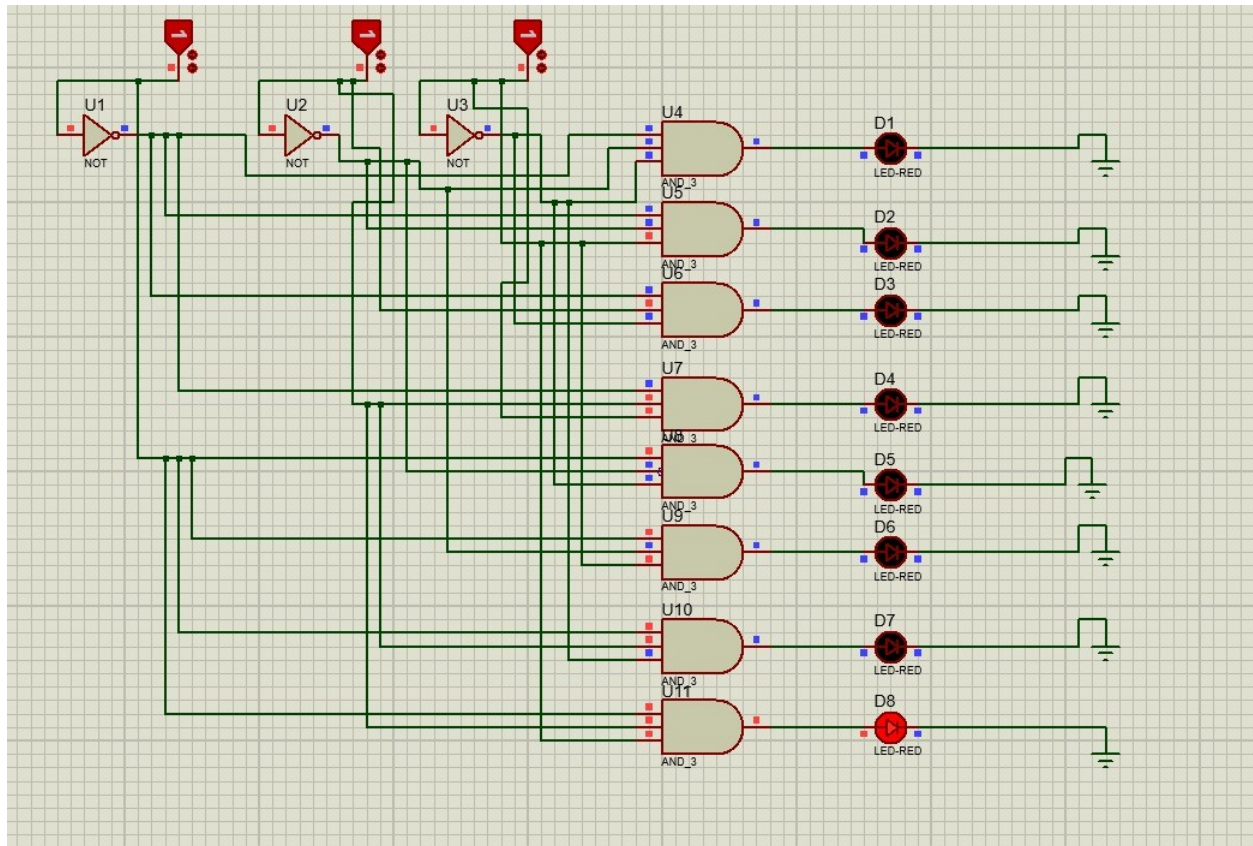

Up and Down

